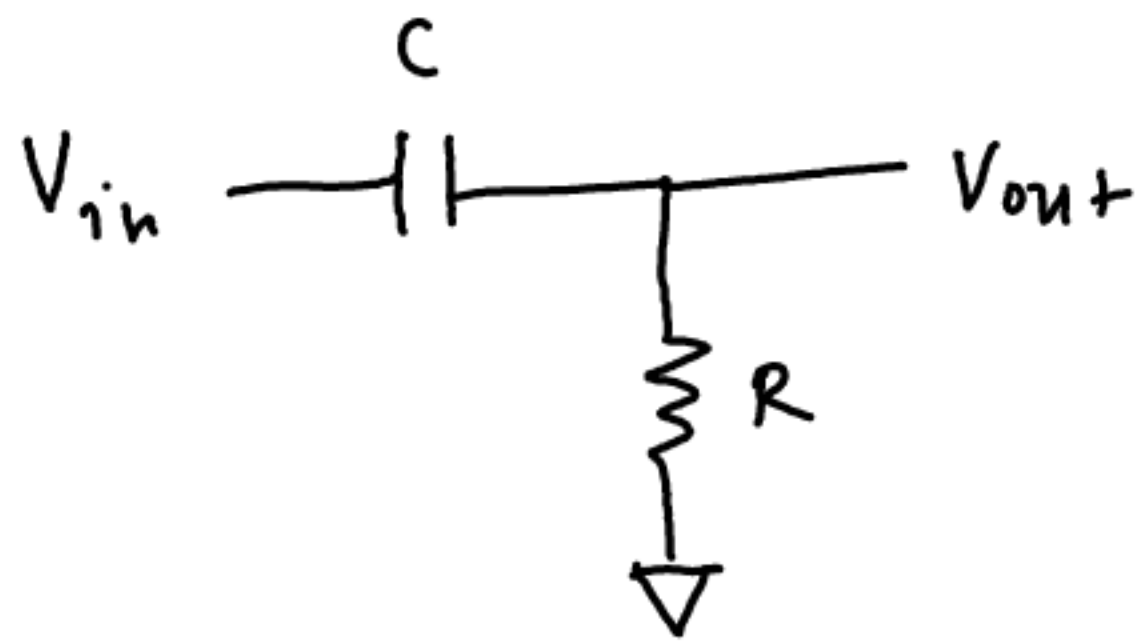


RC filters

In Lab 4 we measured the Gain profile and phase shift from a high-pass filter



Transfer function

$$\frac{V_{out}}{V_{in}} = \frac{z_2}{z_1 + z_2}$$



$$= \frac{z_R}{z_C + z_R}$$

$$\frac{V_{out}}{V_{in}} = \frac{R}{-j/\omega C + R}$$

↙

$$G = \left| \frac{V_{out}}{V_{in}} \right|$$
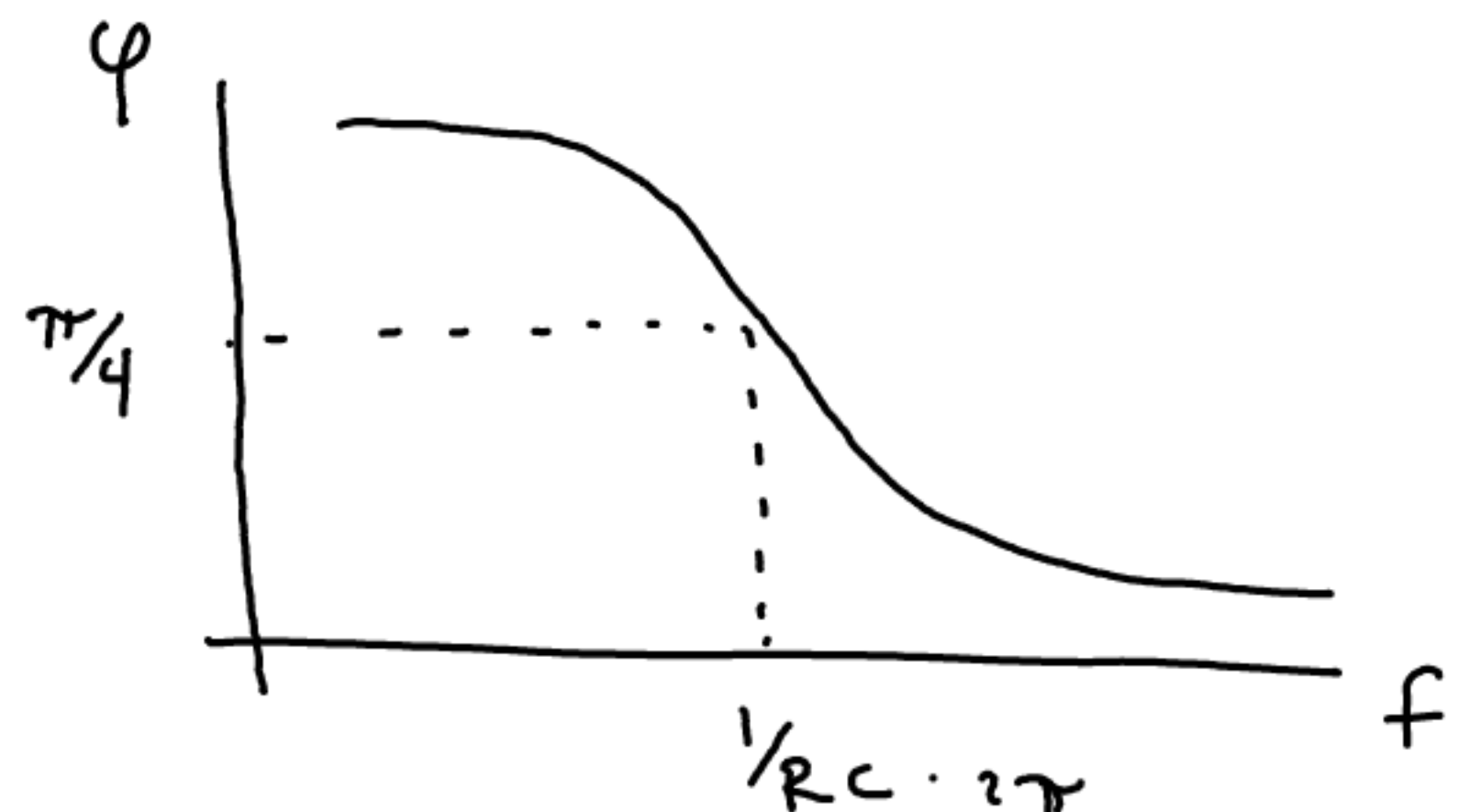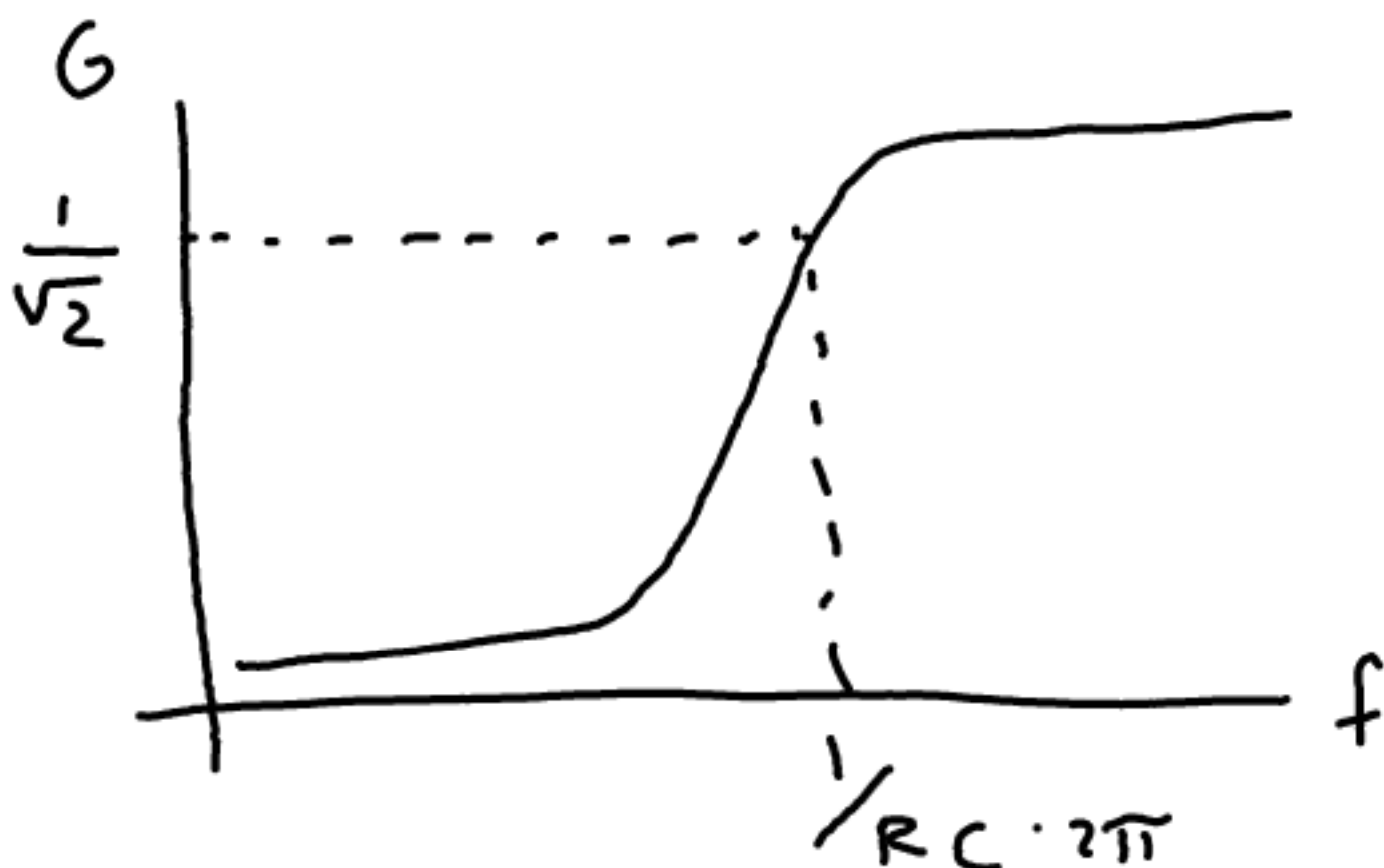
$$\varphi = \tan^{-1} \left(\frac{\text{Im}(V_{out})}{\text{Re}(V_{out})} \right)$$



We can see from the two plots
that high frequencies will pass through
with no effect (close to unity Gain and zero
phase shift) while low frequencies will
get heavily attenuated.

← reduced in amplitude

There is a special frequency to consider.

The crossover frequency $f_c = \frac{1}{2\pi RC}$

This is where $\phi = 45^\circ$

$$G = \frac{1}{\sqrt{2}}$$

← Gain is amplitude

Power is G^2

so this is $\frac{1}{2}$ power

or 3 dB reduction


(see end for dB notes)

When we design a filter,
we want our target
frequencies (to pass) to
be at least 10x higher
than f_c .



"one decade away"

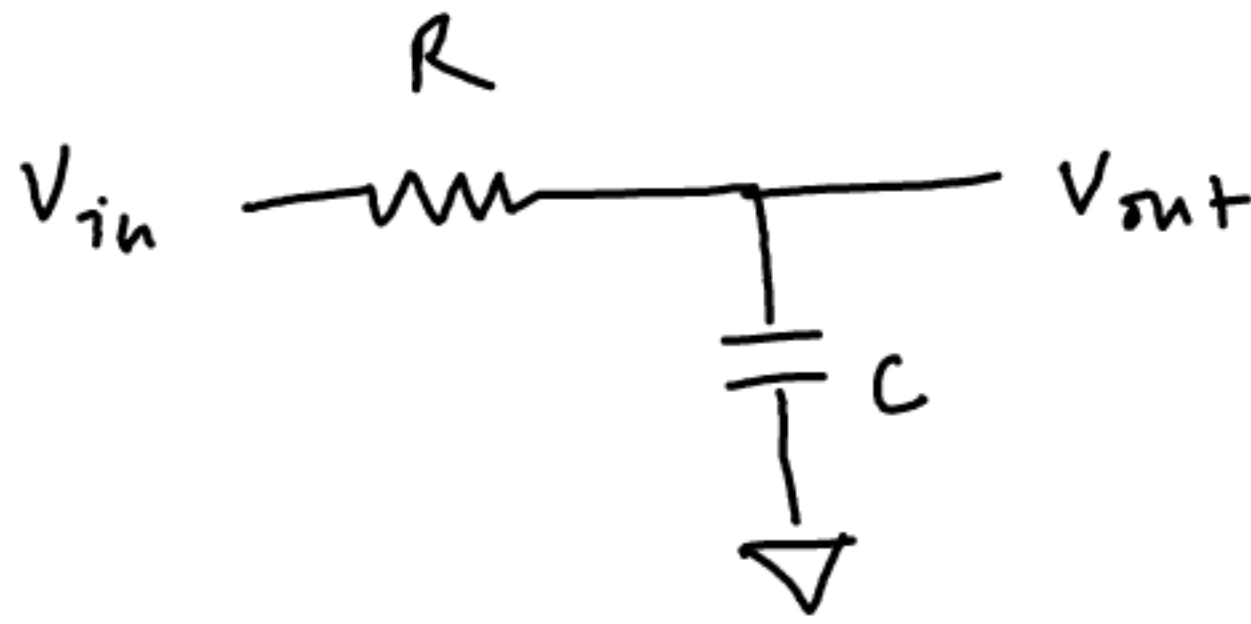Low pass filter is exactly the opposite of the high-pass





$$\frac{V_{out}}{V_{in}} = \frac{-j/\omega C}{R - j/\omega C}$$



$$G = \left| \frac{-j/\omega C}{R - j/\omega C} \right|$$

$$\phi = \tan^{-1}(RC\omega)$$

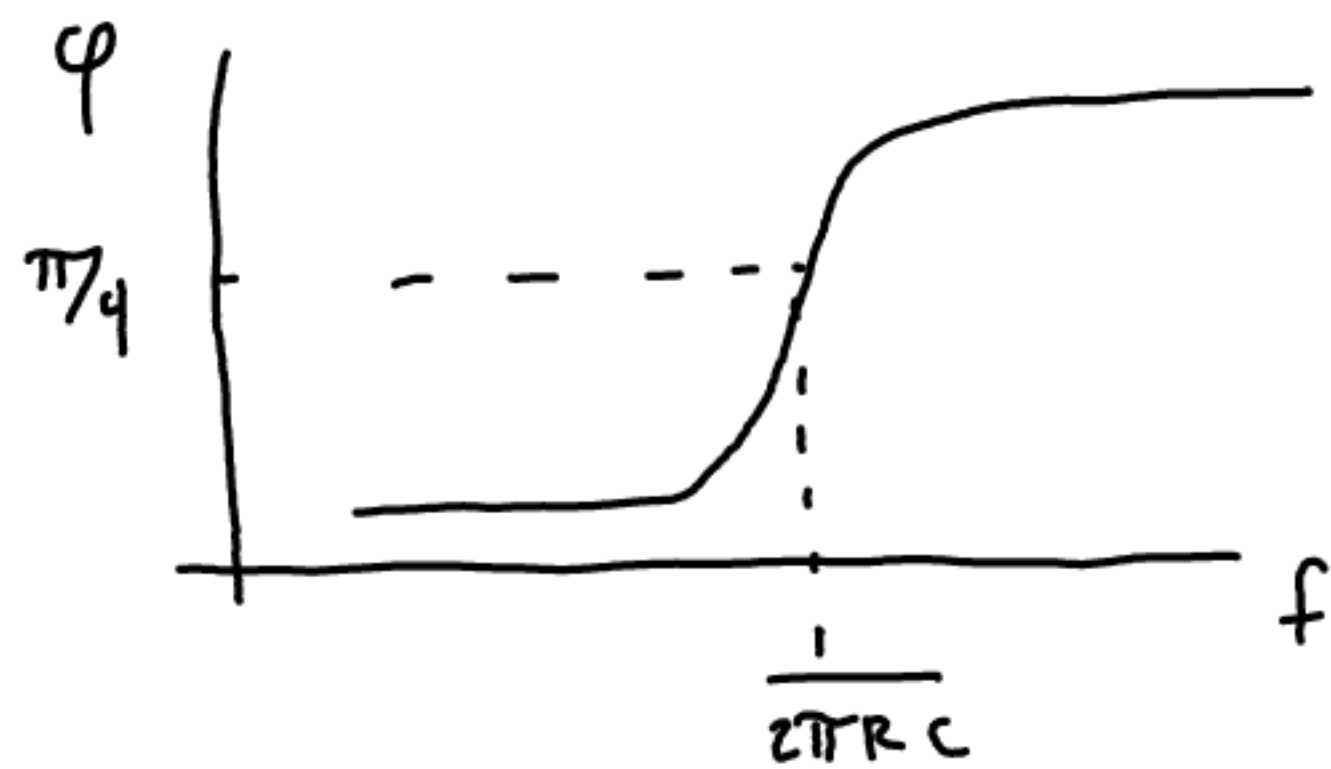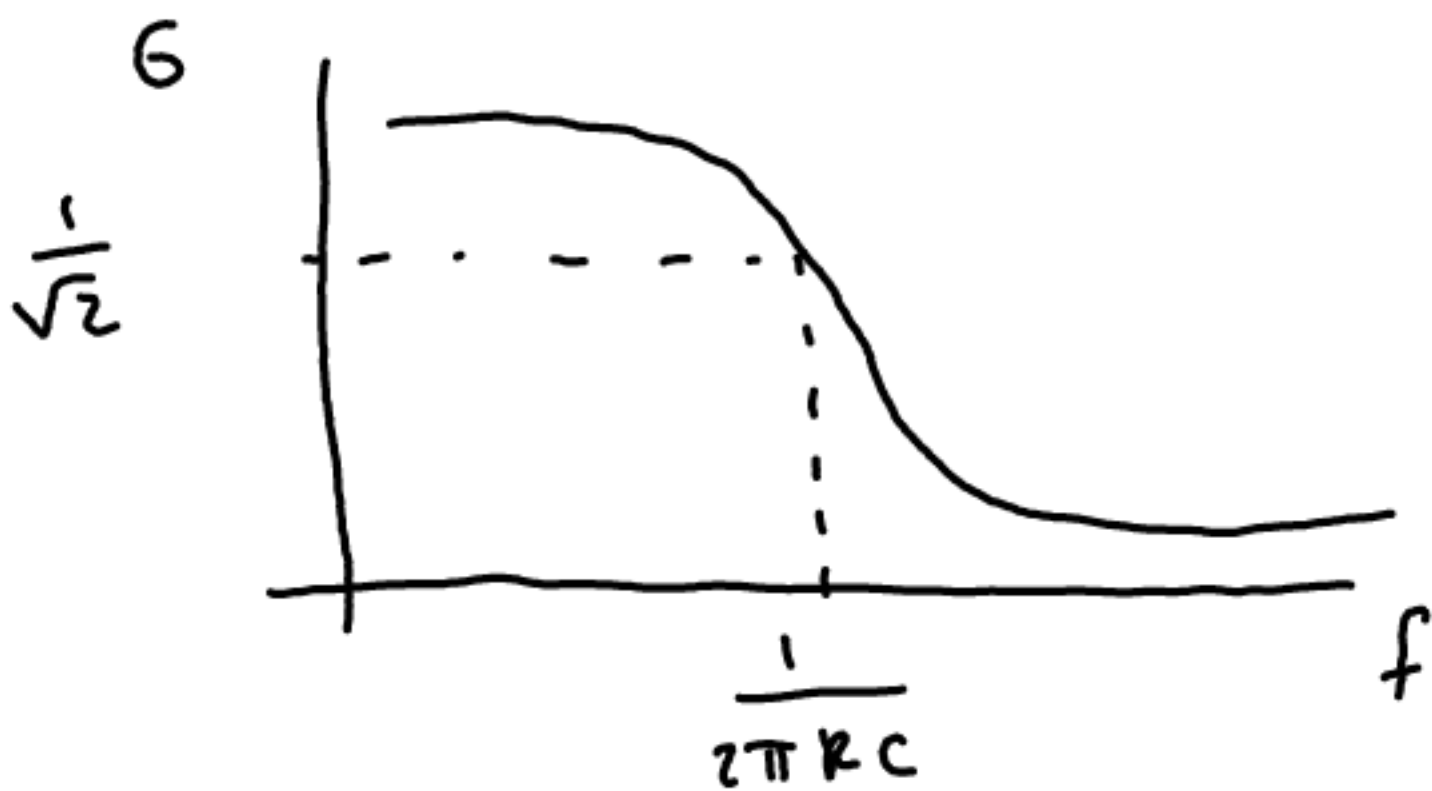

passes low frequency, blocks high frequency.

Note that the crossover frequency


$$f_c = \frac{1}{2\pi RC}$$

has the same form as the high-pass filter.

Band-pass filter

We might want to pass some range (band) of frequencies and exclude everything higher or lower.

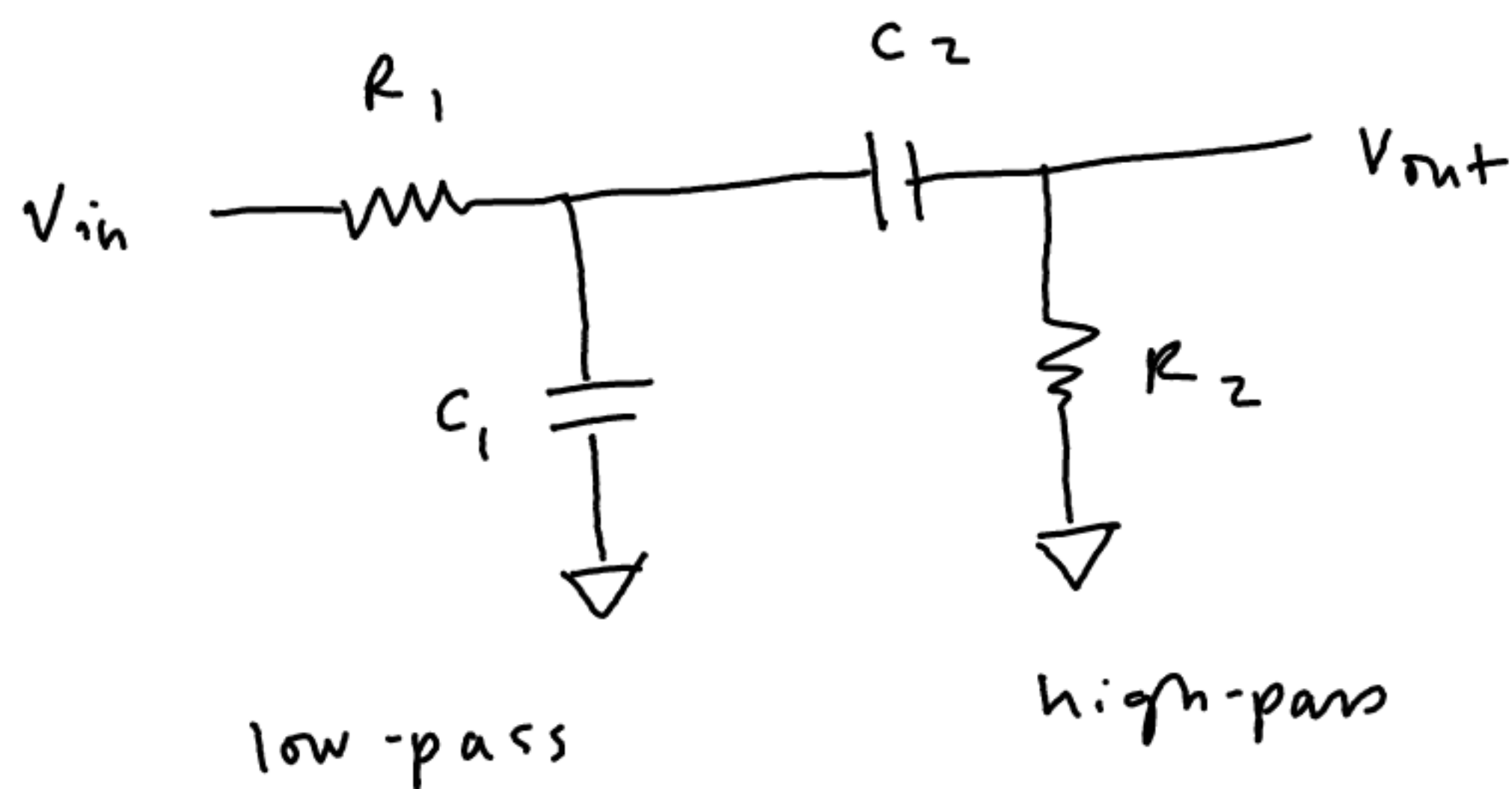We can "simply" combine the high-pass and low-pass filters:



How to choose R, C values:

1. consider source + load impedance for each stage
2. decide on f_c for each stage

1. Impedance matching

Thévenin model says



we typically want
a large V_{Th}



$$R_{load} \gg R_S$$

we should take at
least $\times 10$.

So at every stage,

$$R_{load} \geq 10 R_S$$

2. Low pass f_c should be $10\times$ higher
than band center

High pass f_c should be $10\times$ smaller
than band center

